

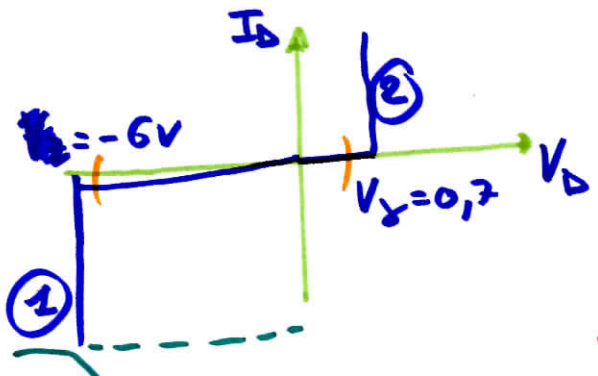




LEZIONI PRIVATE 346/3103392

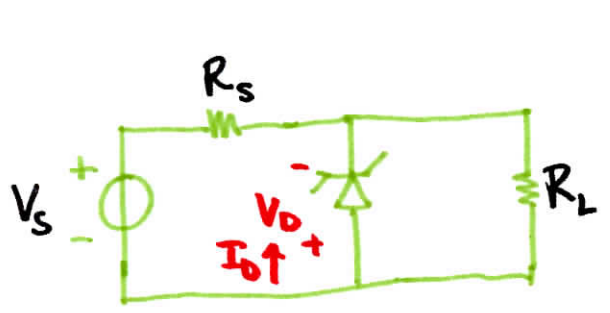

$P_z = V_z I_z$

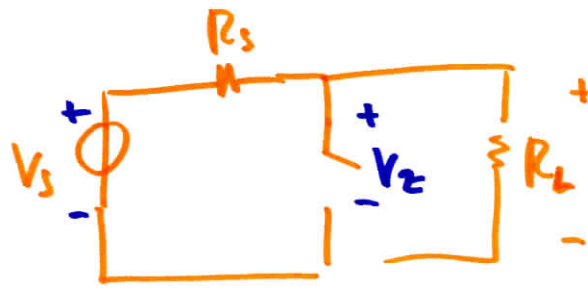

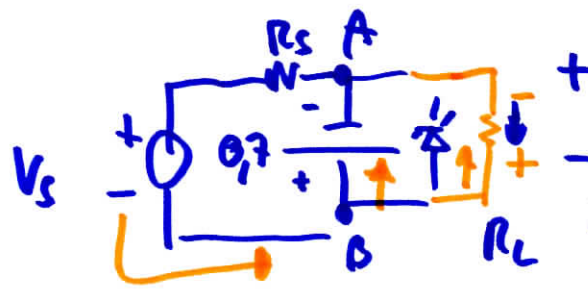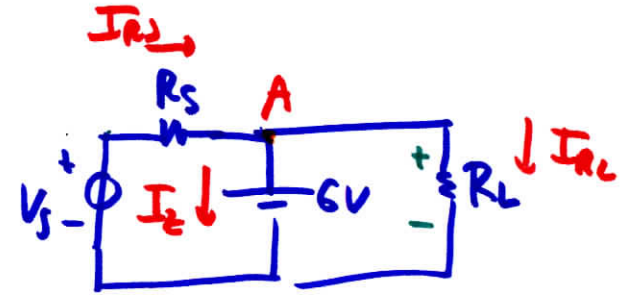$V_{out} = V_s \cdot \frac{R_L}{R_s + R_L} = 6V \quad (V_D = -6V)$




$V_s \cdot \frac{R_L}{R_s + R_L} = -0.7$

$I_{RL} = \frac{-0.7}{R_L}$

$I_{R_s} = I_z + I_{R_L}$

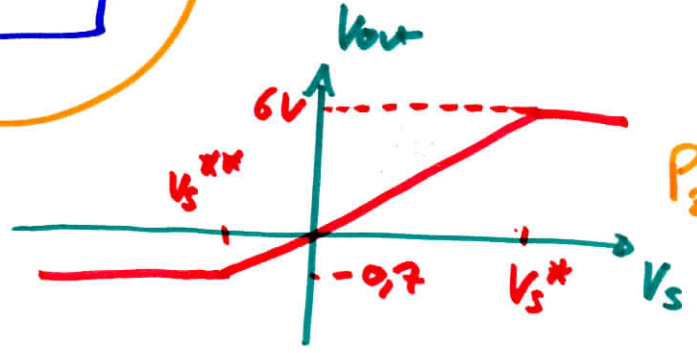$\frac{V_s - V_A}{R_s} = I_z + \frac{6}{R_L}$



$V_{smax} \sim I_{zmax}$

$P_{zmax}$