

LEZIONI PRIVATE 346/3103392


$V_{pp} = 1V$ $R_1 = 1k\Omega$ $R_2 = 5k\Omega$

$A_d = 10^5$


1) $V_d = ?$

$A_d \rightarrow \infty$ $SR = 1V/\mu s$

2) T_{risc}

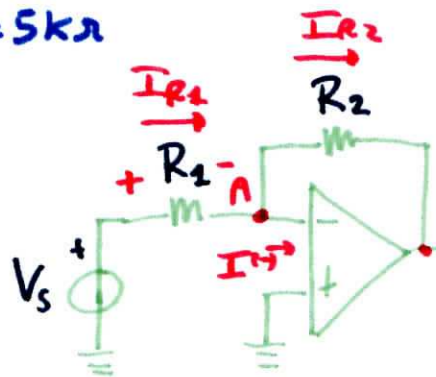

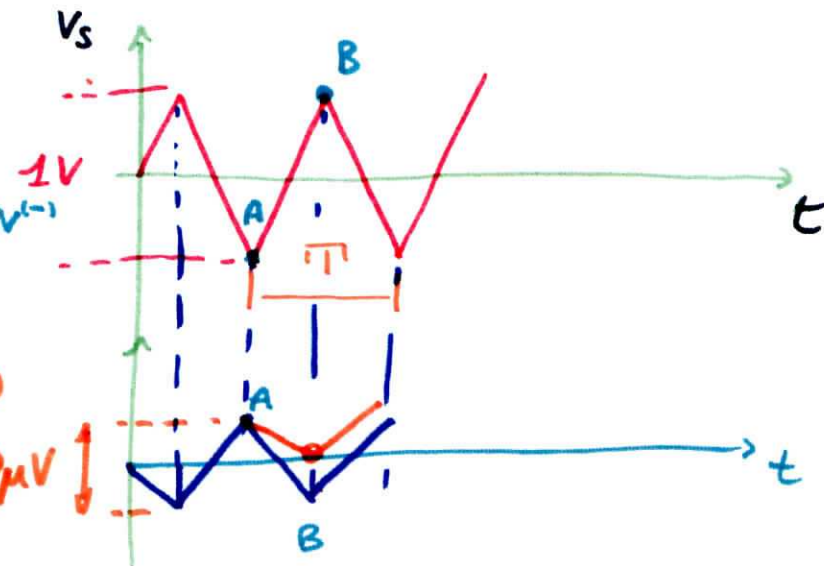$V_{out} = A_d \cdot V_d = -A_d V^{(-)}$
 $V_d = V^{(+)} - V^{(-)}$
 $V_d = -V^{(-)}$



NODO A

$I_{R1} = I_{R2} + I^{(-)} \rightarrow [-A_d V^{(-)}]$
 $\frac{V_s - V^{(-)}}{R_1} = \frac{V^{(-)} - V_{out}}{R_2} \Rightarrow \frac{-V^{(-)}}{V_d} = -V_s \frac{1}{1 + \frac{R_1}{R_2} + A_d \frac{R_1}{R_2}}$

①



$V_d = -V_s \left(\frac{50}{10^6} \right) = V_d$

②

$V_{out} = V_s \left(-\frac{R_2}{R_1} \right)$

$V_{out_{pp}} = 5V$ $SR \geq \frac{\Delta V_{out}}{T/2}$

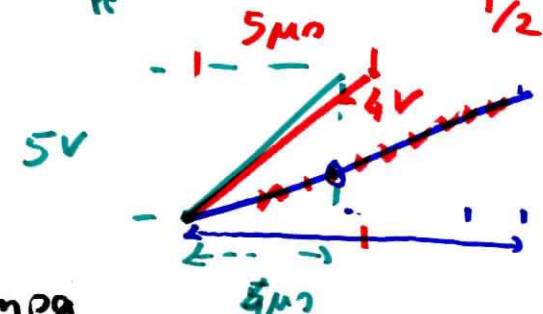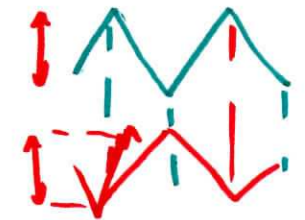$T \geq \frac{2 \cdot \Delta V_{out}}{SR} = \frac{2 \cdot 5V}{\frac{1V}{10^{-6}s}} = 10 \cdot 10^{-6} = 10\mu s$



$T_{risc} = 10\mu s$